

# Vibrations and Controls Homework 9

March 31, 2022

Gabe Morris

```
[1]: # Notebook Preamble
%config ZMQInteractiveShell.ast_node_interactivity = 'all'
import sympy as sp
import numpy as np
import matplotlib.pyplot as plt
from scipy.integrate import odeint

t, s = sp.symbols('t s')


plt.style.use('maroon_ipynb.mplstyle')
```

# Contents

<b>1</b>	<b>Problem 10.4</b>	<b>3</b>
1.1	Given . . . . .	3
1.2	Find . . . . .	3
1.3	Solution . . . . .	3
<b>2</b>	<b>Problem 10.11</b>	<b>5</b>
2.1	Given . . . . .	5
2.2	Find . . . . .	5
2.3	Solution . . . . .	5
	2.3.1 Frequency Response . . . . .	7
<b>3</b>	<b>Problem 10.12 Part B and Part D</b>	<b>10</b>
3.1	Given . . . . .	10
3.2	Find . . . . .	10
3.3	Solution . . . . .	10
	3.3.1 Part B . . . . .	10
	3.3.2 Part D . . . . .	11
<b>4</b>	<b>Problem 10.22</b>	<b>12</b>
4.1	Given . . . . .	12
4.2	Find . . . . .	12
4.3	Solution . . . . .	12
	4.3.1 Part A . . . . .	12
	4.3.2 Part B . . . . .	14

## 1 Problem 10.4

### 1.1 Given

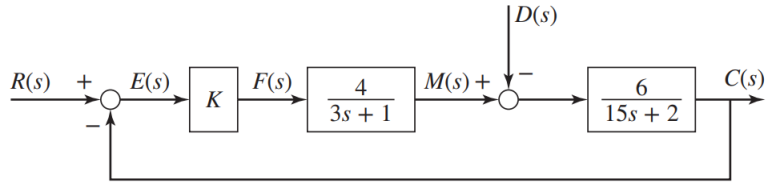

### 1.2 Find

Derive the output  $C(s)$ , error  $E(s)$ , and actuator  $M(s)$  equations for the diagram above and obtain the characteristic polynomial.

### 1.3 Solution

The output of the functions mentioned above may be acquired using algebra of the block diagram.

```
[2]: # Use algebra to determine the functions
K = sp.Symbol('K')
R, E, F, M, D, C, T = [sp.Function(i)(s) for i in ['R', 'E', 'F', 'M', 'D', 'C', 'T']]
eq1 = sp.Eq(E, R - C)
eq1
eq2 = sp.Eq(F, E*K)
eq2
eq3 = sp.Eq(M, F*4/(3*s + 1))
eq3
eq4 = sp.Eq(C, (M - D)*6/(15*s + 2))
eq4
```

[2]:  $E(s) = -C(s) + R(s)$

[2]:  $F(s) = KE(s)$

[2]:  $M(s) = \frac{4F(s)}{3s + 1}$

[2]:  $C(s) = \frac{-6D(s) + 6M(s)}{15s + 2}$

The characteristic polynomial may be determined by solving for  $\frac{C(s)}{R(s)}$ .

```
[3]: subs = eq4.subs([
    (M, eq3.rhs),
    (F, eq2.rhs),
    (E, eq1.rhs),
```

```
(C, T*R)
])
sol = sp.solve(subs, T)[0]
sp.Eq(T, sol)
```

[3]: 
$$T(s) = \frac{6 \cdot (4KR(s) - 3sD(s) - D(s))}{(24K + 45s^2 + 21s + 2) R(s)}$$

$\frac{C(s)}{R(s)}$  may be obtained by setting  $D(s)$  equal to 0.

[4]: `sp.Eq(C/R, sol.subs(D, 0))`

[4]: 
$$\frac{C(s)}{R(s)} = \frac{24K}{24K + 45s^2 + 21s + 2}$$


It is not necessary to try and rewrite  $E(s)$ ,  $M(s)$ , and  $F(s)$  in any other forms. The denominator of the  $\frac{C(s)}{R(s)}$  function above is the characteristic polynomial,

$$45s^2 + 21s + 2 + 24K$$

## 2 Problem 10.11

### 2.1 Given

**Figure 10.4.7** Op-amp implementation of PID action.

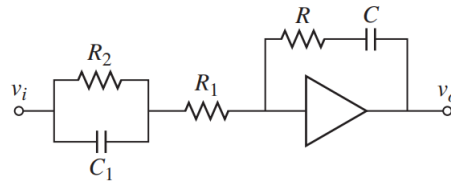

$$\frac{V_o(s)}{V_i(s)} = - \left( K_P + \frac{K_I}{s} + K_D s \right) \frac{1}{\beta R_1 C_1 s + 1}$$

$$K_P = \beta \frac{RC + R_2 C_1}{R_2 C} \quad K_I = \frac{\beta}{R_2 C}$$

$$K_D = \beta R C_1 \quad \beta = \frac{R_2}{R_1 + R_2}$$

### 2.2 Find

- Determine the resistance values to obtain an op-amp PID controller with  $K_P = 10$ ,  $K_I = 1.4$ , and  $K_D = 4$ . The circuit should limit frequencies above 100 rad/s. Take one capacitance to be  $1 \mu F$ .
- Plot the frequency response of the circuit.

### 2.3 Solution

Using the relationships on page 646, we can obtain 4 equations and 4 unknowns.

```
[5]: C, R1, R2, R, C1, beta = sp.symbols('C R_1 R_2 R C_1 \beta')
Vo, Vi = sp.Function('V_o')(s), sp.Function('V_i')(s)
KP = beta*(R*C + R2*C1)/(R2*C)
eq1 = sp.Eq(KP, 10)
KI = beta/(R2*C)
eq2 = sp.Eq(KI, 1.4)
KD = beta*R*C1
eq3 = sp.Eq(KD, 4)
eq4 = sp.Eq(beta, R2/(R1 + R2))
eq1
eq2
eq3
eq4
```

```
[5]: \beta (CR + C_1 R_2)
      CR_2 = 10
```

```
[5]:
```

$$\frac{\beta}{CR_2} = 1.4$$

[5]:  $C_1 R \beta = 4$

[5]:  $\beta = \frac{R_2}{R_1 + R_2}$

Solving the system in terms of  $C$  and  $C_1$ ,

```
[6]: sol = sp.solve([eq1, eq2, eq3, eq4], (R1, R2, R, beta), dict=True)[-1]
     for key, value in sol.items():
         sp.Eq(key, value)
```

[6]:  $R_1 = \frac{0.142857142857143(-2.97728445445476C + 5.0C_1)}{CC_1}$

[6]:  $R_2 = \frac{0.425326350636394}{C_1}$

[6]:  $R = \frac{6.71753079222075}{C}$

[6]:  $\beta = \frac{0.595456890890952C}{C_1}$

Choosing  $C = 1 \cdot 10^{-6} \mu F$ ,

```
[7]: sol2 = {k: v.subs(C, 1e-6) for k, v in sol.items()}
     for key, value in sol2.items():
         sp.Eq(key, value)
```

[7]:  $R_1 = \frac{142857.142857143 \cdot (5.0C_1 - 2.97728445445476 \cdot 10^{-6})}{C_1}$

[7]:  $R_2 = \frac{0.425326350636394}{C_1}$

[7]:  $R = 6717530.79222075$

[7]:  $\beta = \frac{5.95456890890952 \cdot 10^{-7}}{C_1}$

Since  $R_1$  has to be greater than 0, we can use the first equation above to solve for  $C_1$  where  $R_1$  is 0.

```
[8]: C1_lower = sp.solve(sol2[R1], C1)[0]
     C1_lower
```

[8]:  $5.95456890890952 \cdot 10^{-7}$

Notice from the figure above, the natural frequency of the system is  $\frac{1}{\beta R_1 C_1}$ . This means that we need to choose a value for  $C_1$  such that  $\frac{1}{\beta R_1 C_1} \geq 100$ .

```
[9]: C1_upper = sp.solve(1/(sol2[beta]*sol2[R1]*C1) - 100, C1)[0]
     C1_upper
```

[9]:  $6.09793975209791 \cdot 10^{-7}$

Therefore,  $C_1 = 6 \cdot 10^{-7} F$  is a worthy option. The selections for the resistors and capacitors are,

```
[10]: C1_ = 6e-7
      for key, value in sol2.items():
          sp.Eq(key, value.subs(C1, C1_))
      sp.Eq(C1, C1_)
      sp.Eq(C, 1e-6)
```

```
[10]: R1 = 5408.46322505693
```

```
[10]: R2 = 708877.251060657
```

```
[10]: R = 6717530.79222075
```

```
[10]: beta = 0.99242815148492
```

```
[10]: C1 = 6.0 · 10-7
```

```
[10]: C = 1.0 · 10-6
```

### 2.3.1 Frequency Response

Going back to the original transfer function,

```
[11]: %config ZMQInteractiveShell.ast_node_interactivity = 'last_expr'
      T = (-(KP + KI/s + KD*s)*1/(beta*R1*C1*s + 1)).subs(beta, R2/(R1 + R2))
      sp.Eq(Vo/Vi, T.simplify()) # K values are substituted
      T_ = T.subs([
          (R1, sol2[R1].subs(C1, C1_)),
          (R2, sol2[R2].subs(C1, C1_)),
          (R, sol2[R].subs(C1, C1_)),
          (C, 1e-6),
          (C1, C1_)
      ])
      sp.Eq(Vo/Vi, T_)
      w = sp.Symbol(r'\omega')
      T_jw = T_.subs(s, sp.I*w)
      sp.Eq(sp.Function('T')(sp.I*w), T_jw)
```

```
[11]: 
$$\frac{V_o(s)}{V_i(s)} = \frac{-CC_1RR_2s^2 - s(CR + C_1R_2) - 1}{Cs(C_1R_1R_2s + R_1 + R_2)}$$

```

```
[11]: 
$$\frac{V_o(s)}{V_i(s)} = \frac{-4.0s - 10.0 - \frac{1.4}{s}}{0.00322050669649045s + 1}$$

```

```
[11]: 
$$T(i\omega) = \frac{-4.0i\omega - 10.0 + \frac{1.4i}{\omega}}{0.00322050669649045i\omega + 1}$$

```

```
[12]: %config ZMQInteractiveShell.ast_node_interactivity = 'all'
      mag = sp.Abs(T_jw)
      phi = sp.arg(T_jw)
      mag_lamb = sp.lambdify(w, mag, modules='numpy')
      phi_lamb = sp.lambdify(w, phi, modules='numpy')
```

```


w_range = np.linspace(0.1, 500, 15_000)

fig1, ax1 = plt.subplots()
ax1.plot(w_range, mag_lamb(w_range))
ax1.set_xlabel(r'$\omega$')
ax1.set_ylabel(r'$M$')
ax1.set_xscale('log')
ax1.grid(which='minor', ls=':')


fig2, ax2 = plt.subplots()
ax2.plot(w_range, phi_lamb(w_range))
ax2.set_xlabel(r'$\omega$')
ax2.set_ylabel(r'$\phi$')
ax2.set_xscale('log')
ax2.grid(which='minor', ls=':')

plt.show()

```

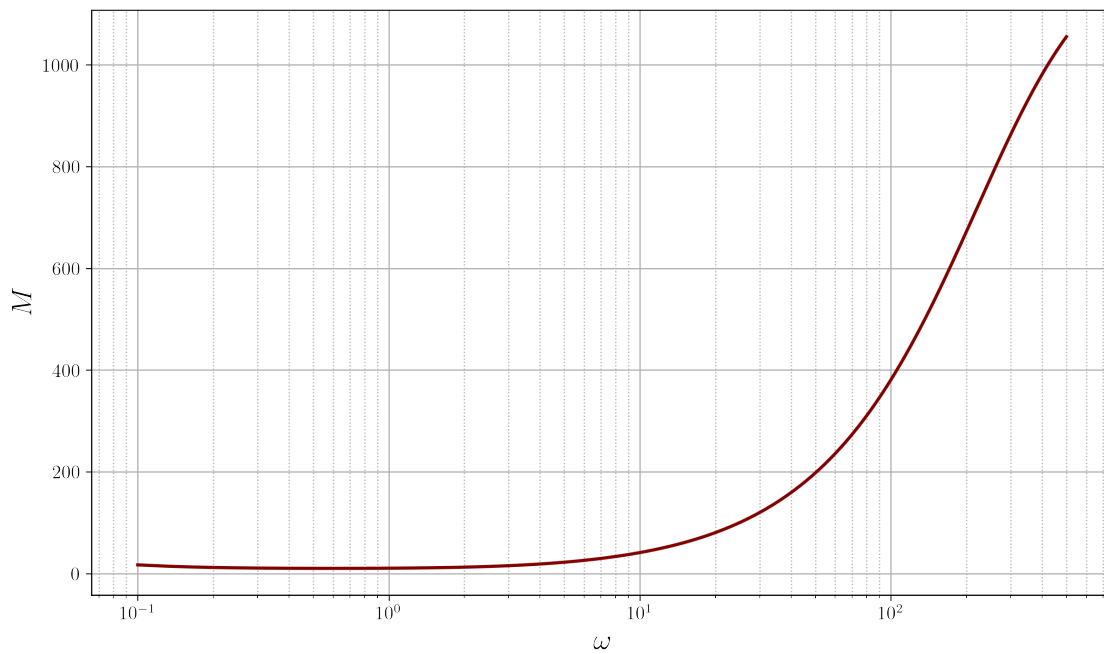



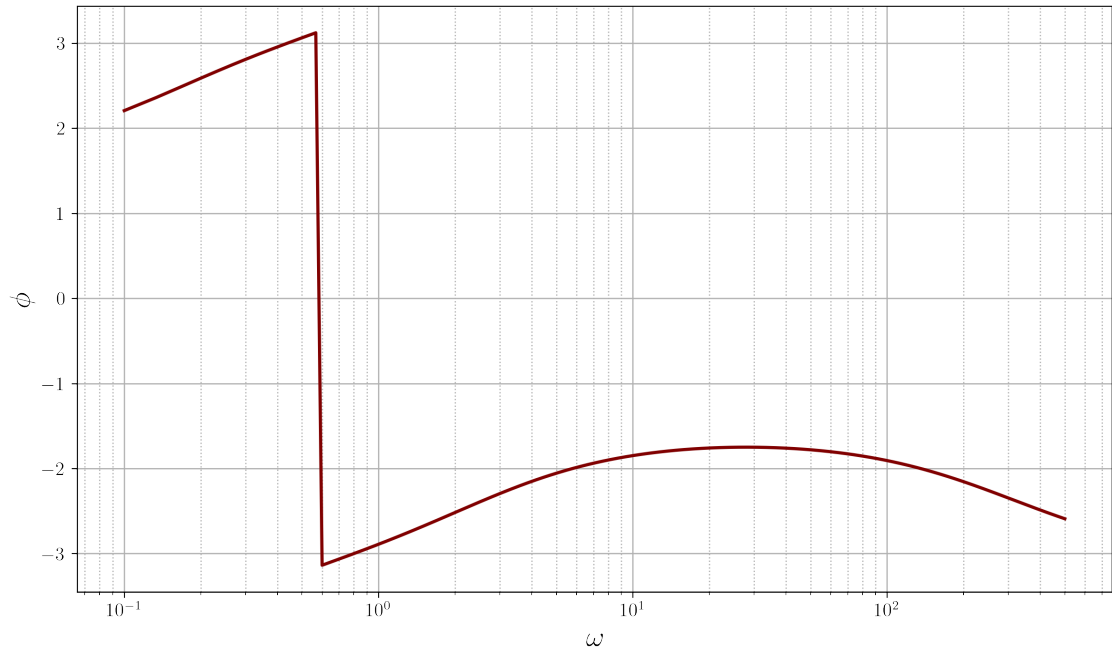

### 3 Problem 10.12 Part B and Part D

#### 3.1 Given

- b.  $\frac{Y(s)}{F(s)} = \frac{8s-5}{10s^2+4s+7}$  and  $f(t) = 8u_s(t)$   
 c.  $\frac{Y(s)}{F(s)} = \frac{5s+8}{s^2+2s-9}$  and  $f(t) = 8u_s(t)$

#### 3.2 Find

The steady state response if possible.

#### 3.3 Solution

The steady state is possible if the system is stable (all roots of the characteristic equation have negative real parts).

##### 3.3.1 Part B

```
[13]: T_b = (8*s - 5)/(10*s**2 + 4*s + 7)
      F = 8/s
      T_b
      poly = sp.fraction(T_b)[1]
      poly
      for root in sp.roots(poly):
          root
```

```
[13]: 8s - 5
      10s^2 + 4s + 7
```

```
[13]: 10s^2 + 4s + 7
```

```
[13]: -1/5 - sqrt(66)i/10
```

```
[13]: -1/5 + sqrt(66)i/10
```

The steady state exists.

```
[14]: lim_b = sp.Limit(s*T_b*F, s, 0)
      sp.Eq(lim_b, lim_b.doit())
```

```
[14]: lim_{s \to 0^+} \left( \frac{8 \cdot (8s - 5)}{10s^2 + 4s + 7} \right) = -\frac{40}{7}
```

### 3.3.2 Part D

```
[15]: T_d = (5*s + 8)/(s**2 + 2*s - 9)
      T_d
      poly = sp.fraction(T_d)[1]
      poly
      for root in sp.roots(poly):
          root
```

```
[15]:  $\frac{5s + 8}{s^2 + 2s - 9}$ 
```

```
[15]:  $s^2 + 2s - 9$ 
```


```
[15]:  $-\sqrt{10} - 1$ 
```

```
[15]:  $-1 + \sqrt{10}$ 
```

The final value theorem does not work because not all roots are negative.

## 4 Problem 10.22

### 4.1 Given

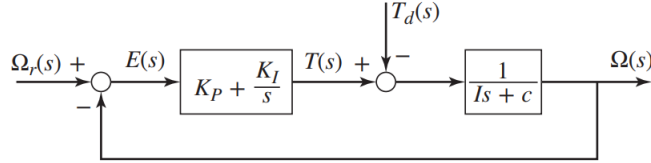

Suppose that  $I = c = 4$  for the PI controller shown above. The performance specifications require that  $\tau = 0.2$ .

### 4.2 Find

- Compute the required gain values for each of the following cases:  $\zeta = 0.707$ ,  $\zeta = 1$ , and a root separation factor of 10.
- Use a computer method to plot the unit step command responses for each of the cases in part (a). Compare the performance of each case.

### 4.3 Solution

The transfer function is,

```
[16]: ohm, ohm_r = sp.Function(r'\Omega')(s), sp.Function(r'\Omega_r')(s)
      KP, KI = sp.symbols('K_P K_I')
      eq = sp.Eq((ohm_r - ohm)*(KP + KI/s)*1/(4*s + 4), ohm)
      eq
      T_s = sp.Function('T')(s)
      sol = sp.solve(eq.subs(ohm, T_s*ohm_r), T_s)[0]
      sp.Eq(ohm/ohm_r, sol)
```

$$[16]: \frac{\left(\frac{K_I}{s} + K_P\right)(-\Omega(s) + \Omega_r(s))}{4s + 4} = \Omega(s)$$

$$[16]: \frac{\Omega(s)}{\Omega_r(s)} = \frac{K_I + K_P s}{K_I + K_P s + 4s^2 + 4s}$$

#### 4.3.1 Part A

$$\tau = \frac{8}{4 + K_P} = 0.2$$

```
[17]: eq1 = sp.Eq(8/(4 + KP), 0.2)
      eq1
      KP_ = sp.solve(eq1, KP)[0]
      sp.Eq(KP, KP_)
```

[17]:

$$\frac{8}{K_P + 4} = 0.2$$

[17]:  $K_P = 36.0$

$$\zeta = \frac{c}{2\sqrt{mk}}$$

```
[18]: # For 0.707
eq2 = sp.Eq((4 + KP_)/(2*sp.sqrt(4*KI)), 0.707)
eq2
KI_707 = sp.solve(eq2, KI)[0]
sp.Eq(KI, KI_707)

# For 1
eq3 = sp.Eq((4 + KP_)/(2*sp.sqrt(4*KI)), 1)
eq3
KI_1 = sp.solve(eq3, KI)[0]
sp.Eq(KI, KI_1)
```

[18]:  $\frac{10.0}{\sqrt{K_I}} = 0.707$

[18]:  $K_I = 200.06041824631$

[18]:  $\frac{10.0}{\sqrt{K_I}} = 1$

[18]:  $K_I = 100.0$

Thus, the gain values are  $K_P = 36$  for  $\zeta = 0.707$  and  $\zeta = 1$  and  $K_I = 200$  for  $\zeta = 0.707$  and  $K_I = 100$  for  $\zeta = 1$ . For the separation factor of 10 (this just means that the other root of the polynomial is some multiple  $10 \cdot \text{other root}$ ), we know that the other root is  $-\frac{1}{\tau} = -5$ . This means that the other root is  $-5 \cdot 10 = -50$ .

```
[19]: poly = (s + 5)*(s + 50)
eq = sp.Eq(poly, poly.expand())
eq
```

[19]:  $(s + 5)(s + 50) = s^2 + 55s + 250$

But in order to compare this characteristic equation with the denominator of the transfer function, the value of  $m$  must be equivalent.

$$4s^2 + 220s + 1000$$

```
[20]: %config ZMQInteractiveShell.ast_node_interactivity = 'last_expr'
eq = sp.Eq(4 + KP, 220)
eq
KP_fact = sp.solve(eq, KP)[0]
sp.Eq(KP, KP_fact)
```

[20]:  $K_P + 4 = 220$

[20]:  $K_P = 216$

Thus,  $K_P = 216$  and  $K_I = 1000$  for the factor of 10 case.

#### 4.3.2 Part B

The responses can be compared by looking at the plot. In the differential equation form with the unit step as the input (just the constant 1 for values greater than 0), the system is,

$$(4s^2 + (4 + K_P)s + K_I)\Omega(s) = (K_I + K_Ps)\frac{1}{s}$$
$$4\ddot{\omega} + (4 + K_P)\dot{\omega} + K_I\omega = K_I$$

The  $K_P$  value on the right-hand side goes away because the inverse laplace transform is technically  $K_P\delta(t)$ , but we are only considering the values greater than 0 ( $K_P\delta(t)$  for  $t > 0$  is 0).

```
[21]: # The best way is to solve numerically
def diffs(x, _, KP__, KI__):
    return [
        x[1],
        1/4*(KI__ - (4 + KP__)*x[1] - KI__*x[0])
    ]

cases = [(KP_, KI_707), (KP_, KI_1), (KP_fact, 1000)]
omega = sp.Function(r'\omega')(t)
time = np.linspace(0, 1.5, 500)
fig, ax = plt.subplots()
for i, case in enumerate(cases):
    KP_value, KI_value = case
    sol = odeint(diffs, (0, 0), time, args=(KP_value, KI_value))
    ax.plot(time, sol[:, 0], label=f'Case {i+1}')
ax.set_xlabel('Time')
ax.set_title('Response')
ax.legend()
plt.show()
```

